


# Problem 1A

HW #2

10520

Ryan St. Pierre

ME 344L

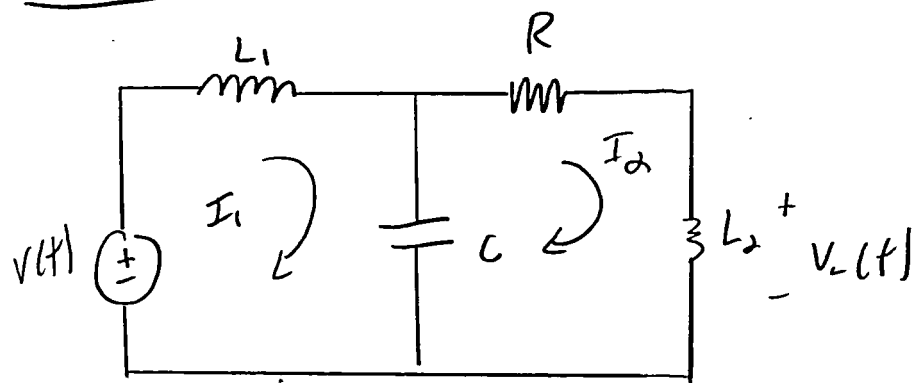

$$I_1: (L_1 s + \frac{1}{Cs}) I_1 - (\frac{1}{Cs}) I_2 = V(s)$$

$$I_2: (\frac{1}{Cs} + R) I_2 - \frac{1}{Cs} I_1 = -V_L(s)$$

Ohm's:  $V_L = I_2 L_2 s$

From Maple


$$\frac{V_L(s)}{V(s)} = \frac{L_2 s}{L_1 L_2 C s^3 + C L_1 R s^2 + L_1 s + L_2 s + R}$$

For  $R=2, C=1/6, L_1=2, L_2=3$

$$\frac{V_L(s)}{V(s)} = \frac{9s}{3s^3 + 2s^2 + 15s + 6}$$

# Problem 1b

ras 20

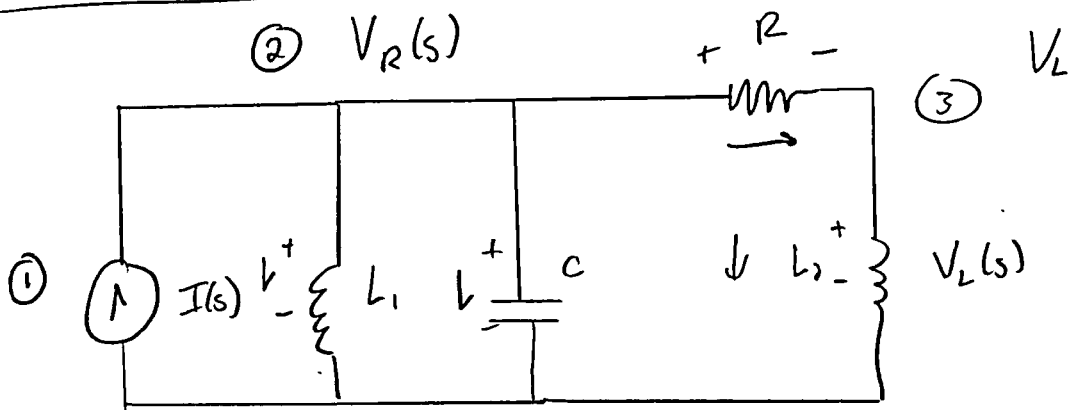

$$\textcircled{1} I(s) = G(s) V_s(s) \quad \text{where} \quad G(s) = \frac{1}{L_1 s}$$

$$I_s(s) = \frac{V_s(s)}{L_1 s}$$

$$\textcircled{2} \frac{V_s}{L_1 s} = \frac{1}{L_1 s} V_R + C s V_R + \frac{1}{R} (V_R - V_L)$$

$$\frac{V_s}{L_1 s} = V_R \left( \frac{1}{L_1 s} + C s + \frac{1}{R} \right) - \frac{1}{R} V_L$$

$$\textcircled{3} \frac{V_R - V_L}{R} = \frac{V_L}{L_2 s}$$

Maple produces the same result as 1a, that is...

$$\frac{V_L(s)}{V(s)} = \frac{L_2 s}{L_1 L_2 C s^3 + C L_1 R s^2 + (L_1 + L_2) s + R}$$


$\Rightarrow$

$$\frac{V_L(s)}{V(s)} = \frac{3s}{s^3 + \frac{2}{3}s^2 + 5s + 6}$$

For  $R=2, C=1/6, L_1=2, L_2=3$

# Problem 2A

as 20

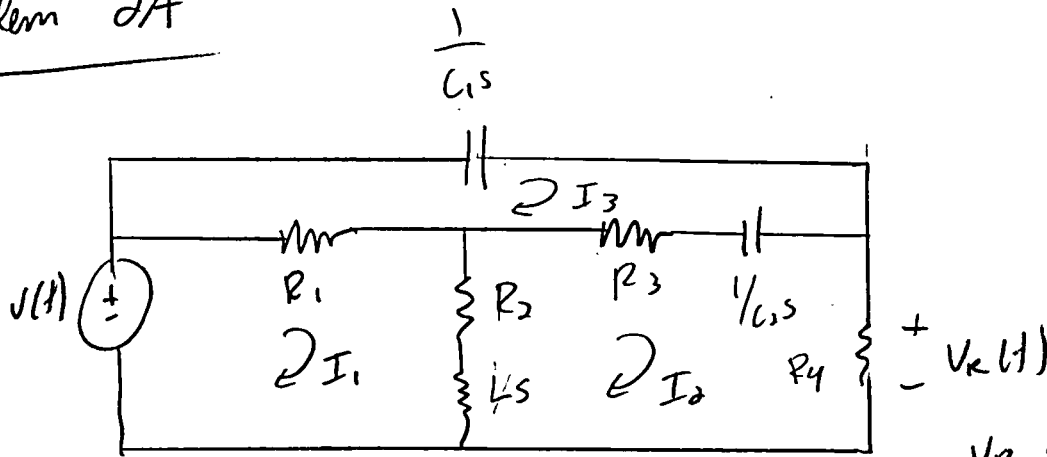

"opposes passive direction"

①  $I_1: (R_1 + R_2 + Ls)I_1 - (R_2 + Ls)I_2 - R_1 I_3 = V(s)$

$I_2: (R_3 + \frac{1}{Cs} + Ls + R_2)I_2 - (R_2 + Ls)I_1 - (R_3 + \frac{1}{Cs})I_3 = -V_R$

$I_3: (\frac{1}{Cs} + R_1 + R_3)I_3 - R_1 I_1 - (R_3 + \frac{1}{Cs})I_2 = 0$

Solving into Maple with given  $C_1, C_2, R_1 \dots$  etc values:

$$\frac{V_R(s)}{V(s)} = \frac{9s^3 + 21s^2 + 12s}{9s^3 + 27s^2 + 25s + 6}$$

(a)

For


# Problem 2b

$V_1, V_2, V_3, V_R$

unknowns

→ need 4 equations

as 20

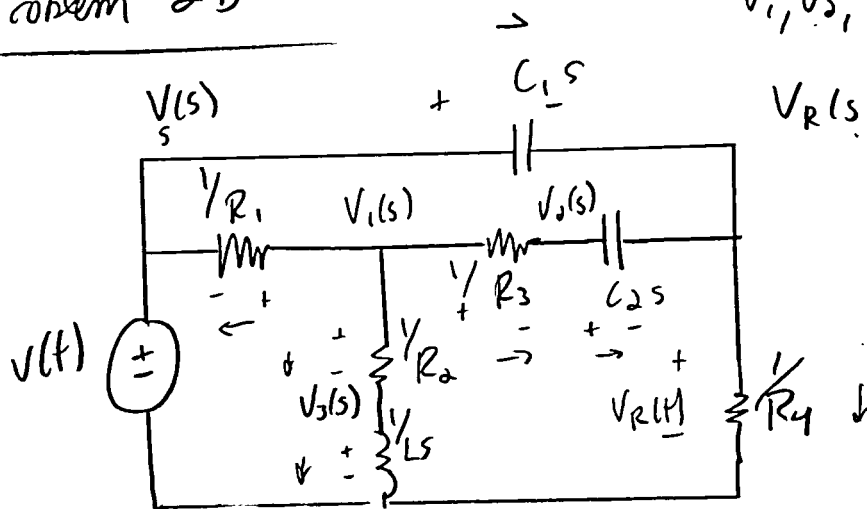

Use

$$\left[ \text{sum of impedances at } n \right] - \sum_{n_i} \left[ \text{impedance shared between } n \text{ \& neighbor } n_i \right] = \left[ \text{current applied at } n \right]$$

$$\textcircled{1} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_1 - \frac{1}{R_1} V_s - \frac{1}{R_3} V_2 - \frac{1}{R_2} V_3 = 0$$

$$\textcircled{2} \left( \frac{1}{R_3} + C_2 s \right) V_2 - \frac{1}{R_3} V_1 - C_2 s V_R = 0$$

$$\textcircled{3} \left( \frac{1}{R_2} + \frac{1}{L s} \right) V_3 - \frac{1}{R_2} V_1 = 0$$


$$\textcircled{4} \left( C_1 s + C_2 s + \frac{1}{R_4} \right) V_R - C_1 s V_1 - C_2 s V_2 = 0$$

Using Maple to solve this, and plugging in the correct values, for  $C_1, C_2, R_1, \dots$  etc results in the following transfer function


$$\frac{V_R(s)}{V(s)} = \frac{9s^3 + 21s^2 + 10s}{9s^3 + 27s^2 + 25s + 6}$$

# Problem 3

ra570

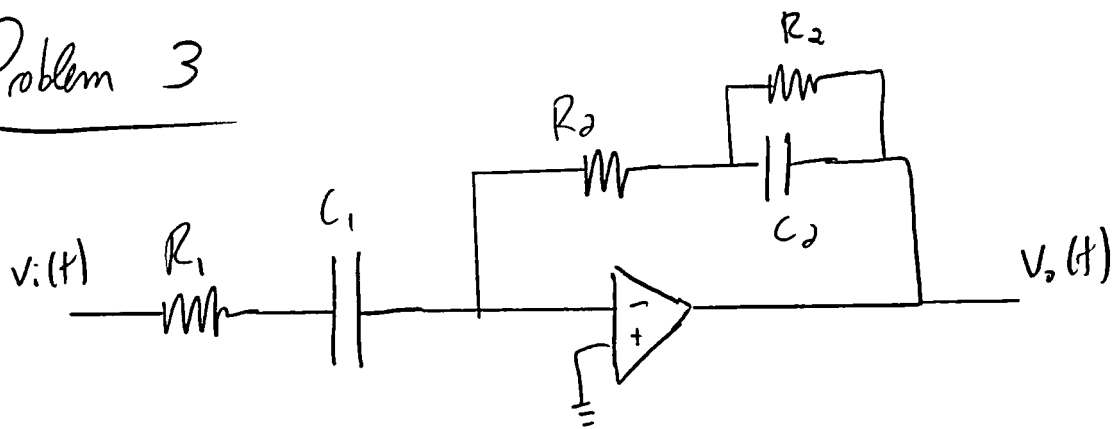

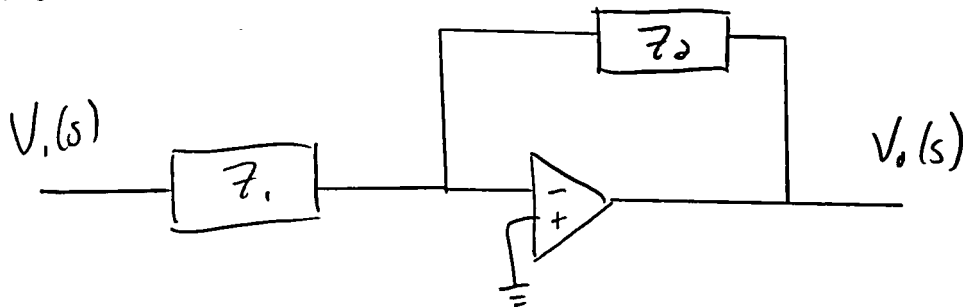This can be simplified to the equivalent inverting amplifier



$$Z_1 = R_1(s) + C_1(s) = R_1 + \frac{1}{Cs}$$

$$Z_2 = R_2(s) + R_2(s) \parallel C_2(s) = R_2 + \frac{1}{Cs + \frac{1}{R_2}} = R_2 + \frac{R_2}{R_2 Cs + 1}$$

$$\frac{V_o(s)}{V_i(s)} = - \frac{Z_2(s)}{Z_1(s)} \quad [\text{given for inverting op amp}]$$

$$= - \frac{R_2 + \frac{R_2}{R_2 Cs + 1}}{R_1 + \frac{1}{Cs}} \cdot \frac{Cs (R_2 Cs + 1)}{Cs (R_2 Cs + 1)}$$

$$= - \frac{R_2 Cs (R_2 Cs + 1) + R_2 Cs}{R_1 Cs (R_2 Cs + 1) + R_2 Cs + 1}$$



### Problem 3 Cont


ms70

$$\frac{V_o(s)}{V_i(s)} = - \frac{R_2 [2C_1 s + R_2 C_1 C_2 s^2]}{R_1 R_2 C_1 C_2 s^2 + R_1 C_1 s + R_2 C_2 s + 1}$$


$$\left| \frac{V_o(s)}{V_i(s)} = -R_2 C_1 s \cdot \frac{R_2 C_2 s + 2}{R_1 R_2 C_1 C_2 s^2 + R_1 C_1 s + R_2 C_2 s + 1} \right|$$

# Problem 4

ras 70

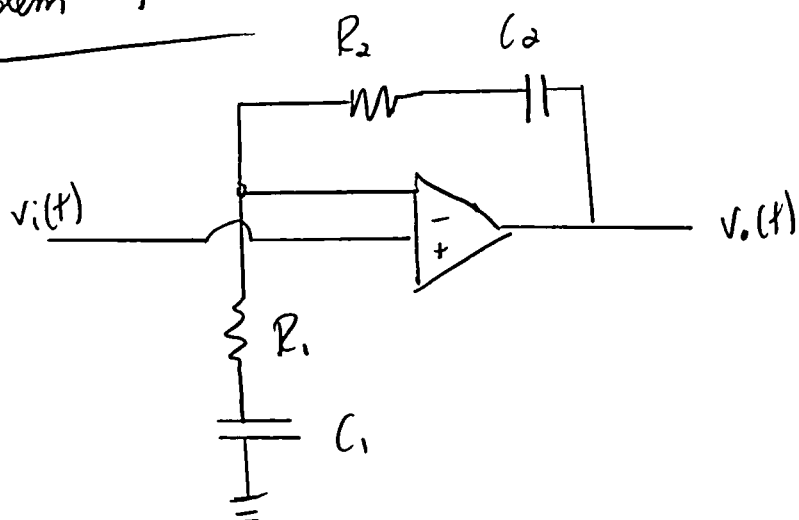

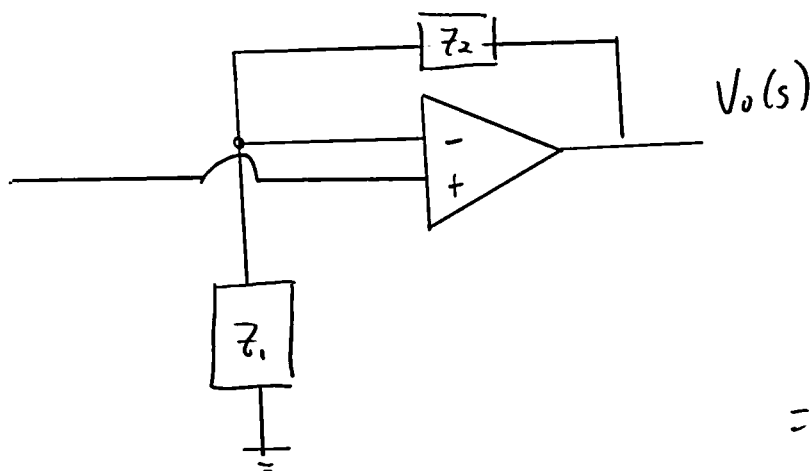This can be converted to the equivalent non-inverting amplifier



$$\frac{V_o(s)}{V_i(s)} = \frac{Z_1(s) + Z_2(s)}{Z_1(s)}$$

$$= \frac{C_1 C_2 s}{C_1 C_2 s} \frac{R_1 + \frac{1}{C_1 s} + R_2 + \frac{1}{C_2 s}}{R_1 + \frac{1}{C_1 s}}$$

$$Z_1(s) = R_1(s) + C_1(s) = R_1 + \frac{1}{C_1 s}$$


$$Z_2(s) = R_2(s) + C_2(s) = R_2 + \frac{1}{C_2 s}$$

$$= \frac{R_1 C_1 C_2 s + C_2 + R_2 C_1 C_2 s + C_1}{R_1 C_1 C_2 s + C_2}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{C_1 C_2 s (R_1 + R_2) + C_1 + C_2}{C_2 (R_1 C_1 s + 1)}$$

# Problem 5

us 20

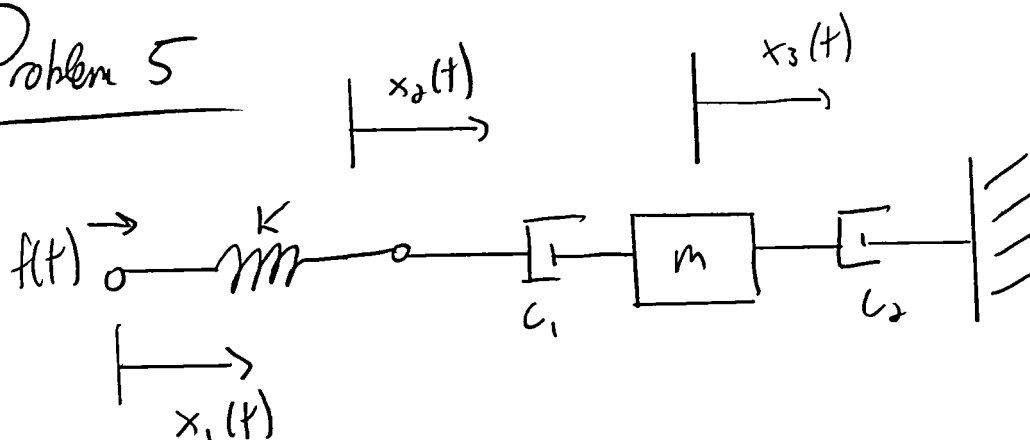

As suggested I will place a zero mass at  $x_2$ . However, I additionally need a zero mass at the coordinate  $x_1$  (which I defined). I believe I need this because the force  $f(t)$  acts on the spring, not directly at  $x_2(t)$ .

$$(1) \left[ \begin{array}{c} \text{Impedances at} \\ x_1 \end{array} \right] X_1(s) - \left[ \begin{array}{c} \text{impedance between} \\ x_1, x_2 \end{array} \right] X_2(s) - \left[ \begin{array}{c} \text{Impedance} \\ x_1, x_3 \end{array} \right] X_3(s) = F(s)$$

$$K X_1(s) - K X_2(s) = F(s)$$

$$(2) \left[ \begin{array}{c} \text{Impedance} \\ x_1, x_2 \end{array} \right] X_1(s) + \left[ \begin{array}{c} \text{Impedance at} \\ x_2 \end{array} \right] X_2(s) - \left[ \begin{array}{c} \text{Impedance} \\ x_2, x_3 \end{array} \right] X_3(s) = 0$$

$$-K X_1(s) + (K + c_1 s) X_2(s) - (c_1 s) X_3(s) = 0$$

$$(3) - \left[ \begin{array}{c} \text{Impedance} \\ x_1, x_3 \end{array} \right] X_1(s) - \left[ \begin{array}{c} \text{Impedance} \\ x_2, x_3 \end{array} \right] X_2(s) + \left[ \begin{array}{c} \text{Impedance} \\ x_3 \end{array} \right] X_3(s) = 0$$

$$- (c_1 s) X_2(s) + (c_1 s + c_2 s + M s^2) X_3(s) = 0$$

→



# Problem 5 cont

ms 20

$$\begin{bmatrix} K & -K & 0 \\ -K & K+c_1s & -c_1s \\ 0 & -c_1s & c_1s+c_2s+Ms^2 \end{bmatrix} \begin{bmatrix} x_1(s) \\ x_2(s) \\ x_3(s) \end{bmatrix} = \begin{bmatrix} F(s) \\ 0 \\ 0 \end{bmatrix}$$

Let  $A = K$ ,  $B = K+c_1s$ ,  $C = -c_1s$ ,  $D = (c_1+c_2)s+Ms^2$

$$\begin{bmatrix} A & -A & 0 \\ -A & B & C \\ 0 & C & D \end{bmatrix} \begin{bmatrix} x_1(s) \\ x_2(s) \\ x_3(s) \end{bmatrix} = \begin{bmatrix} F(s) \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} x_1(s) \\ x_2(s) \\ x_3(s) \end{bmatrix} = \begin{bmatrix} A & -A & 0 \\ -A & B & C \\ 0 & C & D \end{bmatrix}^{-1} \begin{bmatrix} F(s) \\ 0 \\ 0 \end{bmatrix}$$

↙

$$\begin{bmatrix} A & -A & 0 \\ -A & B & C \\ 0 & C & D \end{bmatrix}^{-1} ?$$

Minors

Cofactors

$$\begin{bmatrix} BD-C^2 & -AD & -AC \\ -AD & AD & AC \\ -AC & AC & AB-A^2 \end{bmatrix} \rightarrow \begin{bmatrix} BD-C^2 & AD & -AC \\ AD & AD & -AC \\ -AC & -AC & AB-A^2 \end{bmatrix}$$


Adjunct

$$\begin{bmatrix} BD-C^2 & AD & -AC \\ AD & AD & -AC \\ -AC & -AC & AB-A^2 \end{bmatrix} \rightarrow$$
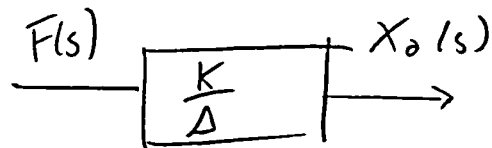
# Problem 5 cont

ms20

$$\begin{bmatrix} A & -A & 0 \\ -A & B & C \\ 0 & C & D \end{bmatrix}^{-1} = \frac{1}{\Delta} \text{ adjoint}$$



$$\Delta = A \begin{vmatrix} B & C \\ C & D \end{vmatrix} + A \begin{vmatrix} -A & C \\ 0 & D \end{vmatrix} + 0$$

$$= A(BD - C^2) + A(-AD)$$

$$\begin{bmatrix} x_1(s) \\ x_2(s) \\ x_3(s) \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} BD - C^2 & AD & -AC \\ AD & AD & -AC \\ -AC & -AC & AB - A^2 \end{bmatrix} \begin{bmatrix} F(s) \\ 0 \\ 0 \end{bmatrix}$$

$$X_2(s) = \frac{1}{\Delta} (AD) F(s)$$

$$\frac{X_2(s)}{F(s)} = \frac{1}{\Delta} (AD) = \frac{AD}{A(BD - C^2) - A^2 D} = \frac{D}{BD - C^2 - AD}$$

$$= \frac{(c_1 + c_2)s + ms^2}{(k + c_1 s)(c_1 + c_2)s + c_1^2 s^2 - k[(c_1 + c_2)s + ms^2]}$$

$$= \frac{c_1 + c_2}{(k + c_1 s)(c_1 + c_2) + c_1^2 s - k[(c_1 + c_2)s + ms^2]}$$

$$= \frac{c_1 + c_2 + mk s}{k(c_1 + c_2) + c_1 s(c_1 + c_2) + c_1^2 s - k(c_1 + c_2) - mk s}$$

13/

Problem 5 cont

$$\frac{X_0(s)}{F(s)} = \frac{C_1 + C_2 + MKs}{C_1 s (C_1 + C_2) + C_1^2 s - MKs}$$

$$\frac{X_2(s)}{F(s)} = \frac{C_1 + C_2 + MKs}{s [C_1^2 + C_1 C_2 + C_1^2 - MK]} = \frac{C_1 + C_2 + MKs}{s [2C_1^2 + C_1 C_2 - MK]}$$

$$\frac{X_0(s)}{F(s)} = \frac{C_1 + C_2 + MKs}{s [2C_1^2 + C_1 C_2 - MK]}$$


I have simplified this out fully. A cleaner representation is

$$\frac{X_0(s)}{F(s)} = \frac{K}{\Delta}$$

where  $\Delta = \begin{vmatrix} k & -K & 0 \\ -K & k + C_1 s & -C_1 s \\ 0 & -C_1 s & C_1 s + C_2 s + Ms^2 \end{vmatrix}$

# Problem 6

rus 20

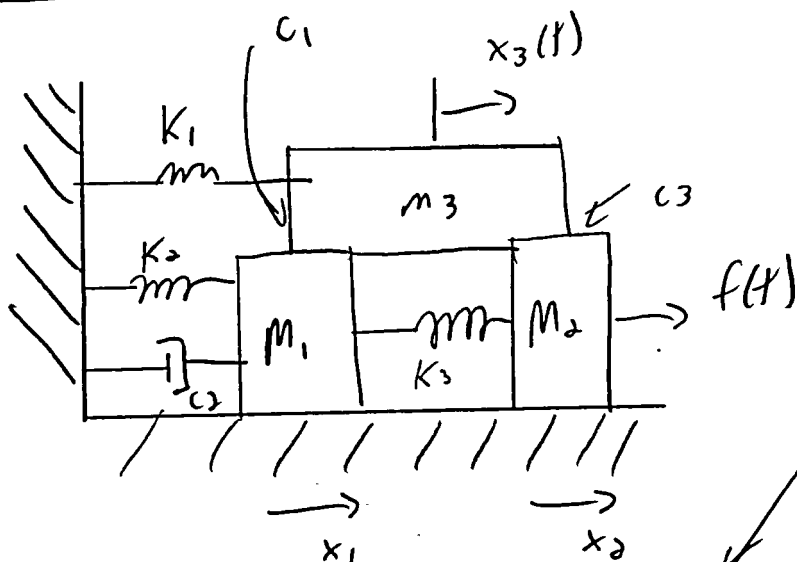

3 degrees of freedom

assume function of  $s$

$$M_1: [M_1 s^2 + (C_1 + C_2)s + K_2 + K_3]X_1 - K_3 X_2 - C_1 X_3 = 0$$


$$M_2: [M_2 s^2 + C_3 s + K_3]X_2 - K_3 X_1 - C_3 X_3 = F(s)$$

$$M_3: [M_3 s^2 + (C_1 + C_3)s + K_1]X_3 - C_1 X_1 - C_3 X_2 = 0$$

I found the transfer function for this problem, as produced by Maple to be long. Thus, I have excluded it here. Please refer to my Maple scripts for the answer.

# Problem 7

us 70

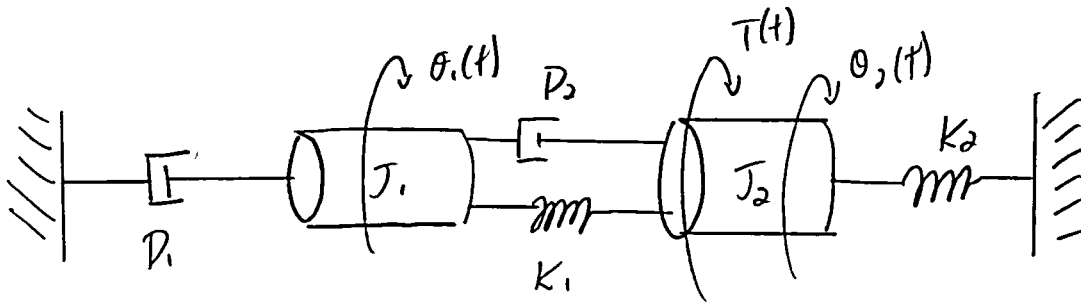

2 degrees of freedom

As done in the book the equations of motion can be done by inspection in the following manner

$$(1) \left[ \begin{array}{c} \text{sum of impedances} \\ \text{connected to} \\ \text{motion at } \theta_1 \end{array} \right] \theta_1(s) - \left[ \begin{array}{c} \text{sum of impedances} \\ \text{between } \theta_1 \text{ and } \theta_2 \end{array} \right] \theta_2(s) = \left[ \begin{array}{c} \text{Torque} \\ \text{applied} \\ \text{to } \theta_1 \end{array} \right]$$

$$(J_1 s^2 + D_1 s + D_2 s + K_1) \theta_1(s) - (D_2 s + K_1) \theta_2(s) = 0$$

$$(2) - \left[ \begin{array}{c} \text{sum of impedances} \\ \text{between } \theta_1 \text{ and} \\ \theta_2 \end{array} \right] \theta_1(s) + \left[ \begin{array}{c} \text{sum of impedances} \\ \text{connected to motion of} \\ \theta_2 \end{array} \right] \theta_2(s) = \left[ \begin{array}{c} \text{Torque applied} \\ \text{at } \theta_2 \end{array} \right]$$


$$- (D_2 s + K_1) \theta_1(s) + (J_2 s^2 + D_2 s + K_1 + K_2) \theta_2(s) = T(s)$$

2 equations of motion are:

$$\left\{ \begin{array}{l} (J_1 s^2 + (D_1 + D_2) s + K_1) \theta_1(s) - (D_2 s + K_1) \theta_2(s) = 0 \\ - (D_2 s + K_1) \theta_1(s) + (J_2 s^2 + D_2 s + K_1 + K_2) \theta_2(s) = T(s) \end{array} \right.$$

# Problem 8

rus20

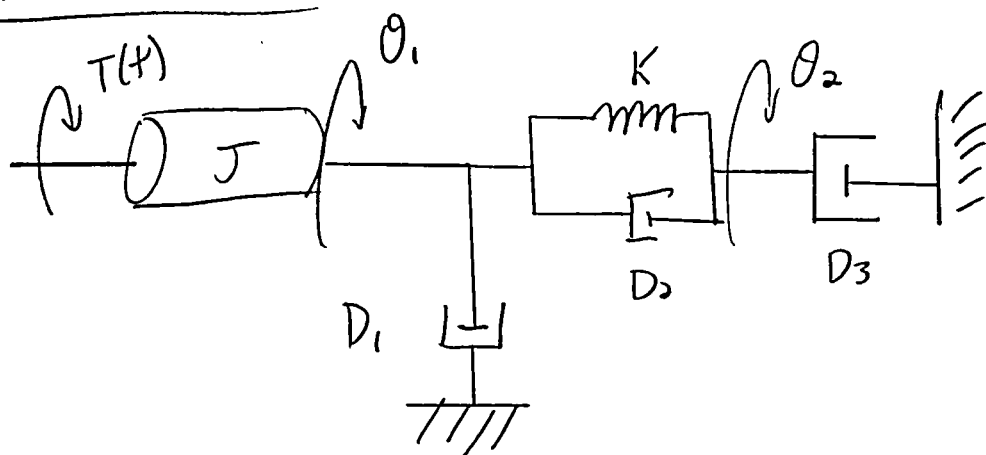

2 degrees of freedom -  
 $\theta_1, \theta_2$  only  
 coordinates needed to  
 describe system


Using inspection method described in Problem 7

$$① (Js^2 + D_1s + D_2s + K)\theta_1(s) - (D_2s + K)\theta_2(s) = T(s)$$

$$② -(D_2s + K)\theta_1(s) + (D_2s + D_3s + K)\theta_2(s) = 0$$

From the pattern observed in the examples in the book I know the solution should be
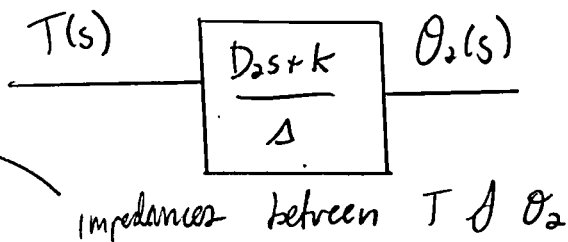
$$\frac{\theta_2(s)}{T(s)} = \frac{D_2s + K}{\Delta}$$



$$\text{where } \Delta = \begin{vmatrix} (Js^2 + (D_1 + D_2)s + K) & -(D_2s + K) \\ -(D_2s + K) & ((D_2 + D_3)s + K) \end{vmatrix}$$

I'll solve the system to show why this is the case:

$$\text{Let } A = (Js^2 + D_1s + D_2s + K)$$

$$B = -(D_2s + K)$$

$$C = (D_2s + D_3s + K)$$

The system can be represented by

$$\begin{bmatrix} A & B \\ B & C \end{bmatrix} \begin{bmatrix} \theta_1(s) \\ \theta_2(s) \end{bmatrix} = \begin{bmatrix} T(s) \\ 0 \end{bmatrix} \rightarrow$$

# Problem 8 cont

cas70

$$\begin{bmatrix} A & B \\ B & C \end{bmatrix} \begin{bmatrix} \theta_1(s) \\ \theta_2(s) \end{bmatrix} = \begin{bmatrix} T(s) \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} \theta_1(s) \\ \theta_2(s) \end{bmatrix} = \begin{bmatrix} A & B \\ B & C \end{bmatrix}^{-1} \begin{bmatrix} T(s) \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} \theta_1(s) \\ \theta_2(s) \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} C & -B \\ -B & A \end{bmatrix} \begin{bmatrix} T(s) \\ 0 \end{bmatrix} \quad \text{where } \Delta = \begin{vmatrix} A & B \\ B & C \end{vmatrix}$$

$$\begin{bmatrix} \theta_1(s) \\ \theta_2(s) \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} CT(s) \\ -BT(s) \end{bmatrix}$$

$$\theta_2(s) = \frac{-BT(s)}{\Delta}$$

$$\frac{\theta_2(s)}{T(s)} = \frac{-B}{\Delta} = - \frac{(D_2s+k)}{\Delta} = \frac{D_2s+k}{\Delta}$$

$$\boxed{\frac{\theta_2(s)}{T(s)} = \frac{D_2s+k}{\Delta}}$$

$$\Delta = \begin{vmatrix} A & B \\ B & C \end{vmatrix} = AC - B^2 = (Js^2 + (D_1 + D_2)s + k)((D_2 + D_3)s + k) - (D_2s + k)^2$$

↗  
squared so I can drop  
the negative